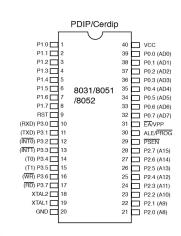
8051 Microcontroller: External Memory Interfacing



Virendra Singh

Computer Architecture and Dependable Systems Lab
Department of Electrical Engineering
Indian Institute of Technology Bombay
http://www.ee.iitb.ac.in/~viren/


E-mail: viren@ee.iitb.ac.in

FE-309: Microprocessors







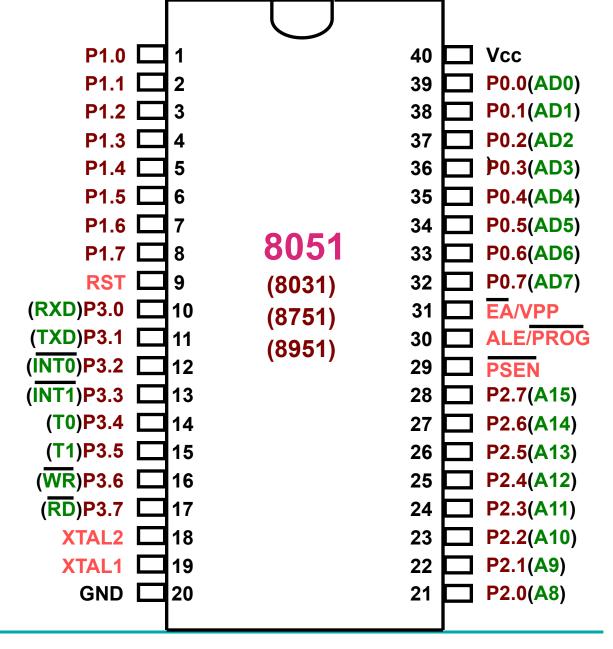




CADSL

2

8051 Interfacing With External Memory

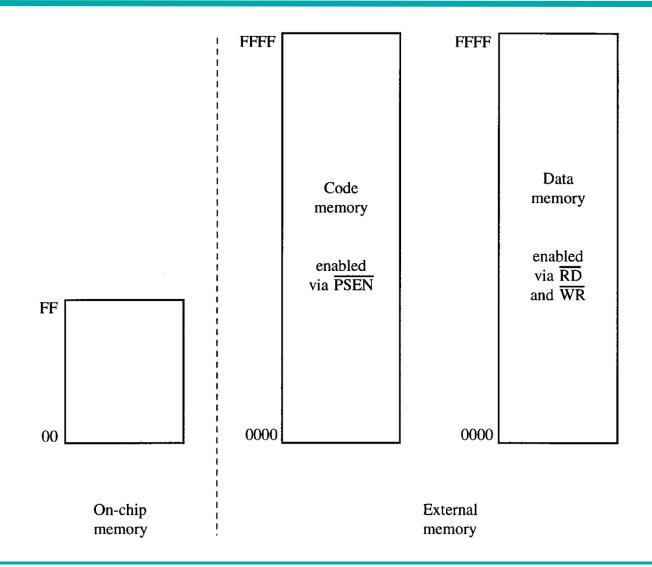





8051 Interfacing With External ROM


PSEN

$$8051$$
EA = V_{CC}


$$8052$$
 EA = V_{CC}

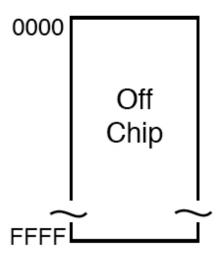

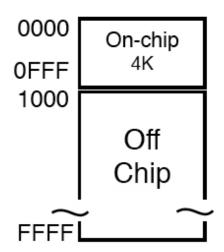

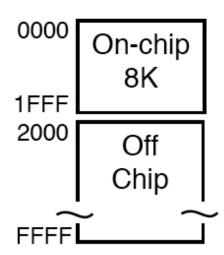


Reading ROM

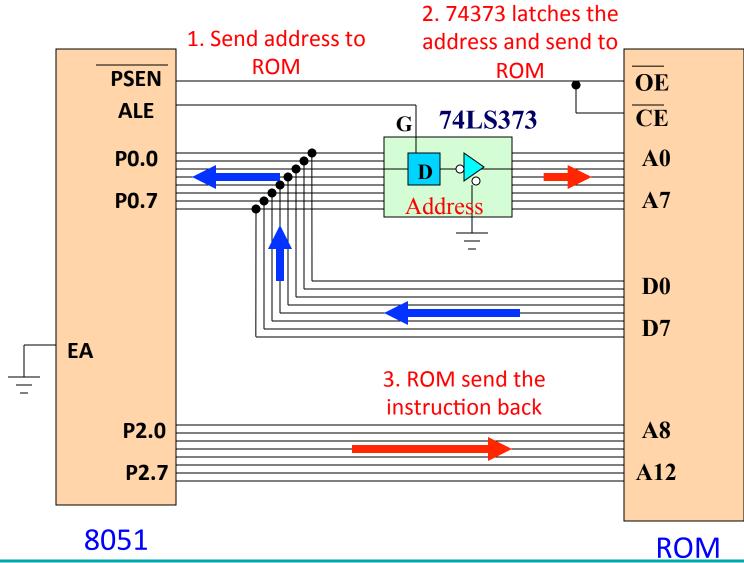




Timing Diagram

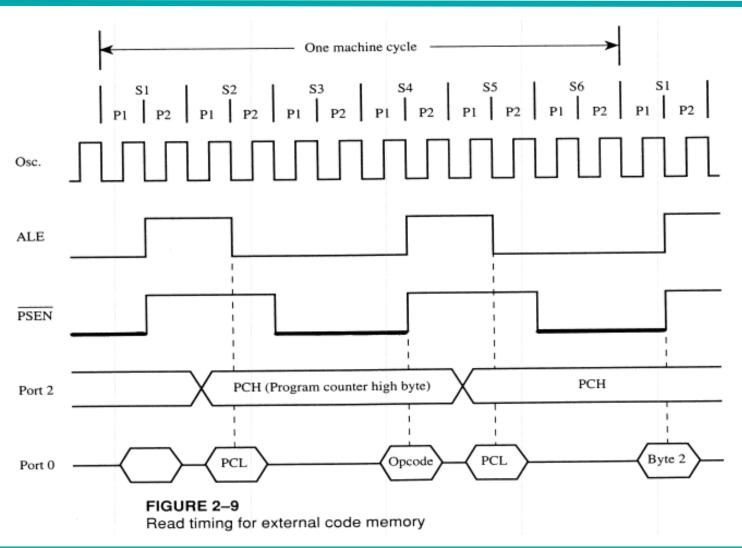




8051 Interfacing With External ROM

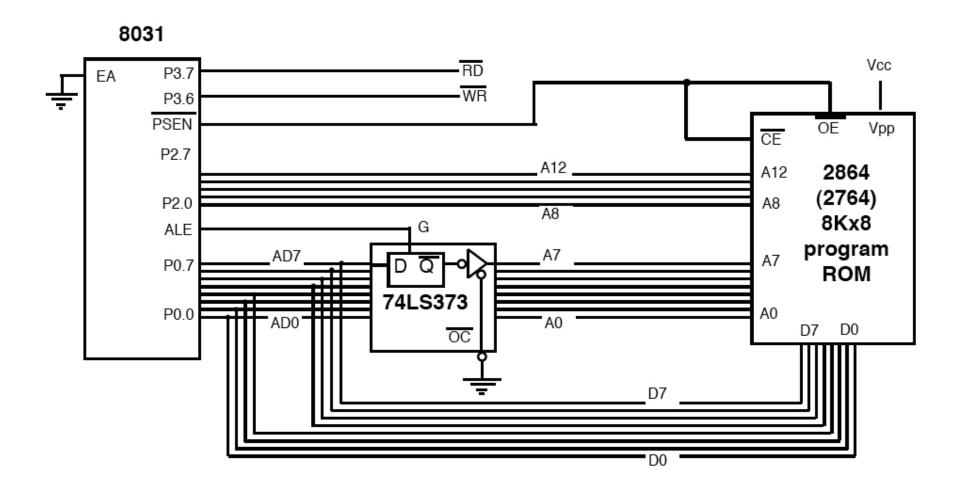




Data memory space

8051

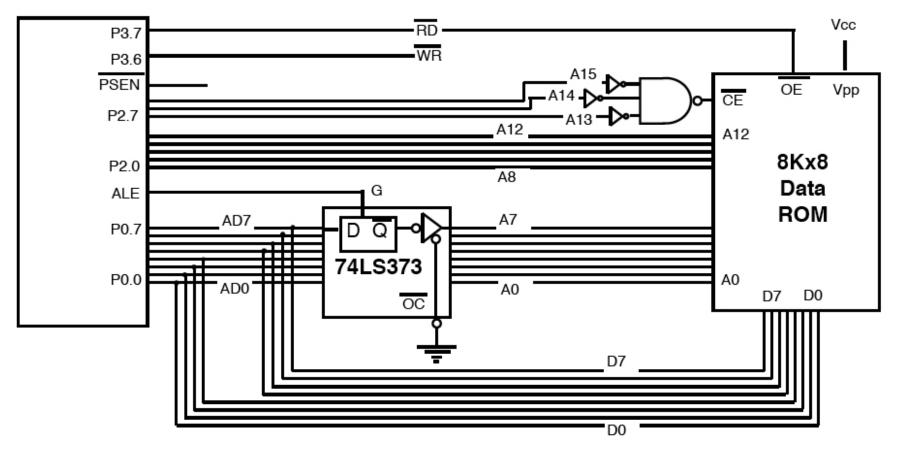




MOVX instruction

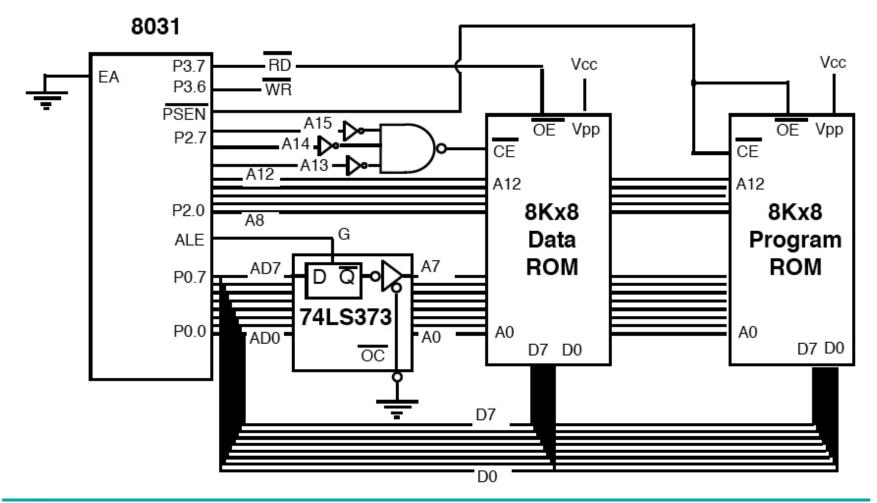




Timing for MOVX instruction

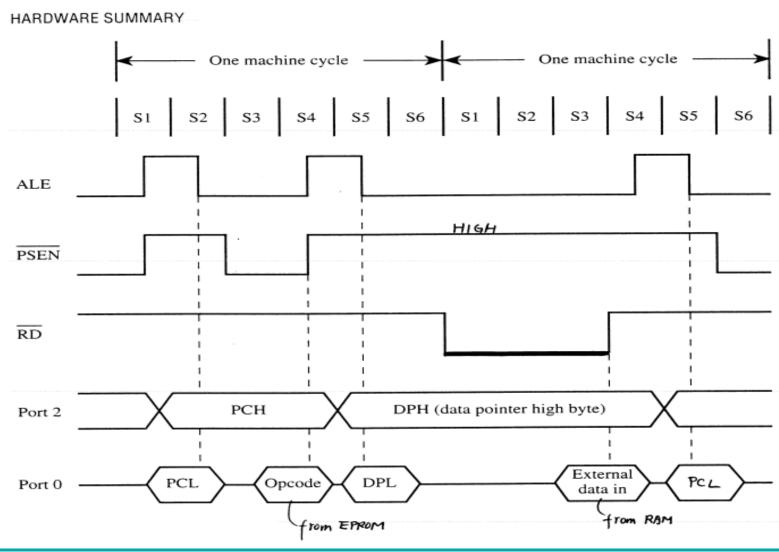



MOVX instruction for external RAM data


8051

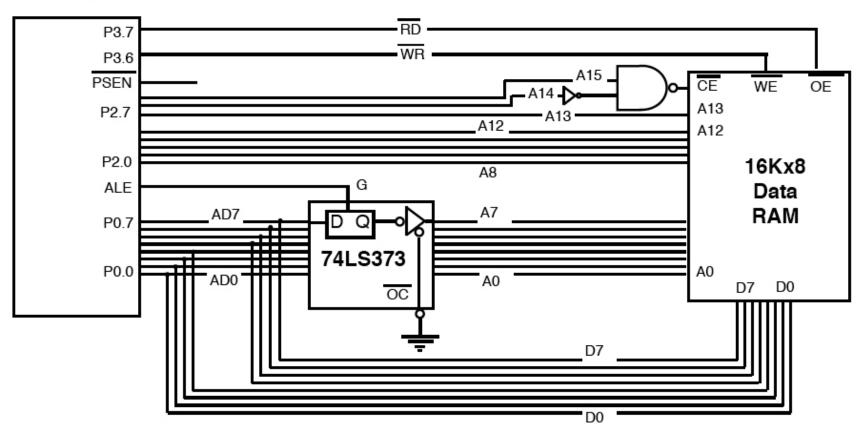






A single external ROM for code and data

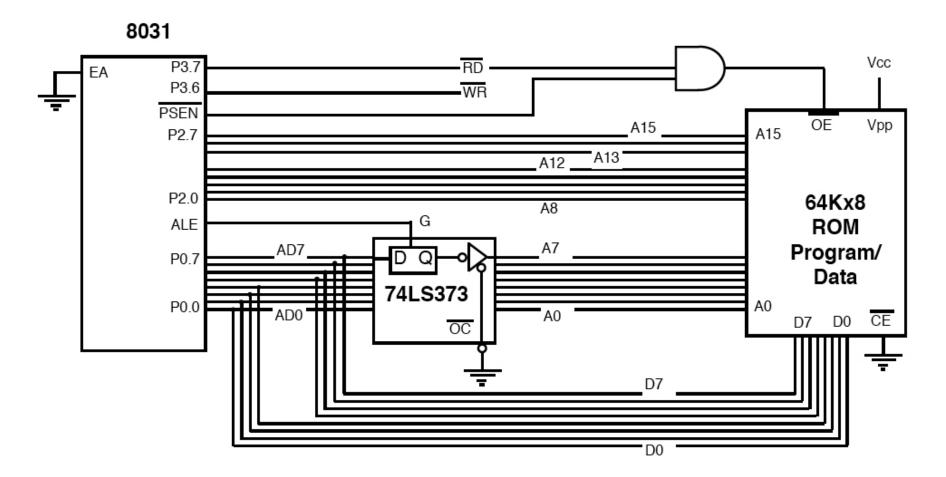






8051 Data/Program Memory Space

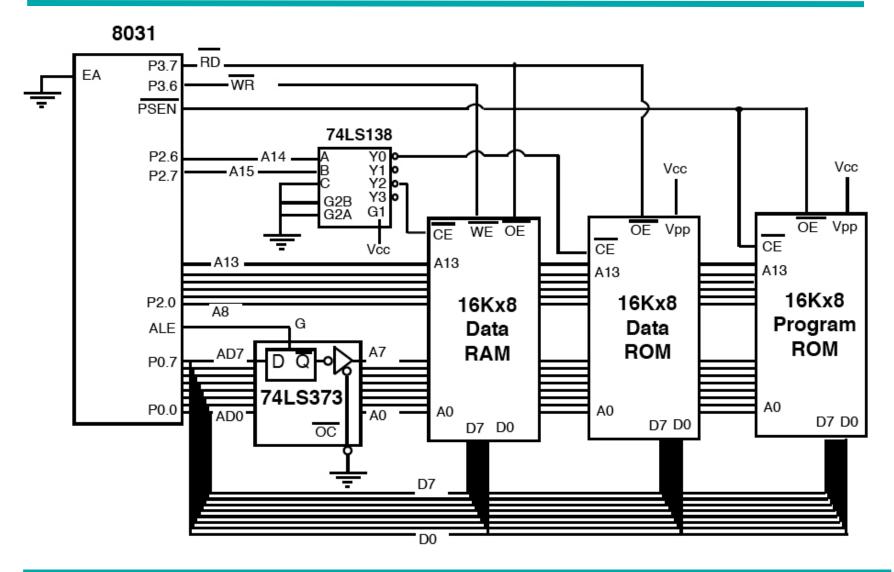



Interfacing to large external memory

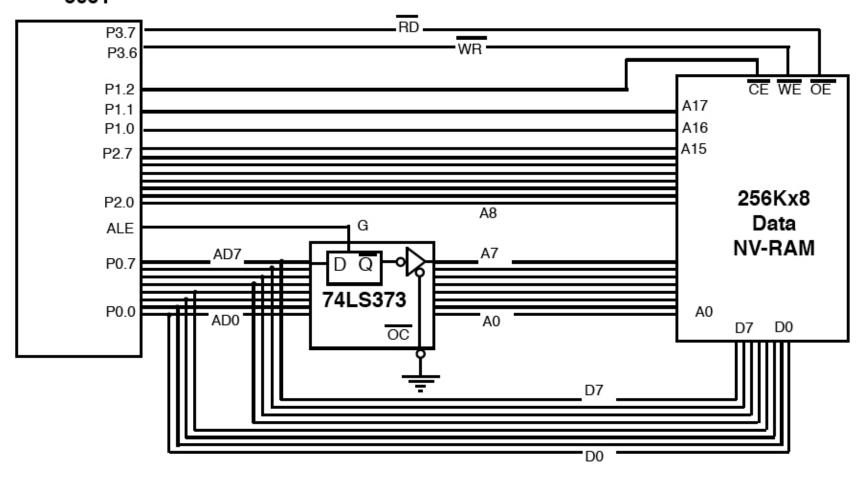



Little or Big: Where to Start?

- Byte ordering: Where is the first byte?
- Big-endian: IBM,
 SPARC, Mororola
- Little-endian: Intel, DEC
- Supporting both: MIPS, PowerPC

Number 0x5678

Little-endian E		Big-endian	
5		8	
		7	
7		6	
8		5	
	5 6 7	5 6 7	5 8 6 7 7





Thank You



