

RISC Design

Single Cycle Implementation

Virendra Singh

Computer Architecture and Dependable Systems Lab

Department of Electrical Engineering

Indian Institute of Technology Bombay

<http://www.ee.iitb.ac.in/~viren/>

E-mail: viren@ee.iitb.ac.in

EE-309: Microprocessors



Lecture 30 (05 Oct 2015)

CADSL

Overview of DLX

- ❖ Simple instructions, all 32 bits wide
- ❖ Very structured, no unnecessary baggage
- ❖ Only three instruction formats

R	op	rs1	rs2	rd	funct
I	op	rs1	rd	16 bit address	
J	op	26 bit address			

- ❖ Rely on compiler to achieve performance




Where Does It All Begin?


- *Program counter (PC).*
- PC contains the memory address of the next instruction to be executed.
- In the beginning, PC contains the address of the memory location where the program begins.



Where is the Program?

 

How Does It Run?

 

Datapath and Control

- **Datapath:** Memory, registers, adders, ALU, and communication buses. Each step (fetch, decode, execute) requires communication (data transfer) paths between memory, registers and ALU.
- **Control:** Datapath for each step is set up by control signals that set up dataflow directions on communication buses and select ALU and memory functions. Control signals are generated by a control unit consisting of one or more finite-state machines.



Example Instruction Set: Mini-DLX (DLX Subset)

MIPS Instruction – Subset

❖ Arithmetic and Logical Instructions

➤ add, sub, xor, and, sll

❖ Memory reference Instructions

➤ lw, sw

❖ Branch

➤ beq, j




Mini-DLX Instruction Set


ADD Rd, Rs1, Rs2	$Rd \leftarrow Rs1 + Rs2$ (overflow – exception)	R	000_000/ 000_100
SUB Rd, Rs1, Rs2	$Rd \leftarrow Rs1 - Rs2$ (overflow – exception)	R	000_000/ 000_110
AND Rd, Rs1, Rs2	$Rd \leftarrow Rs1 \text{ and } Rs2$	R	000_000/ 001_000
XOR Rd, Rs1, Rs2	$Rd \leftarrow Rs1 \text{ xor } Rs2$	R	000_000/ 001_010
SLL Rd, Rs1, Rs2	$Rd \leftarrow Rs1 \ll Rs2$ (logical) (5 lsb of Rs2 are significant)	R	000_000/ 001_100
LW Rd, Imm (Rs1)	$Rd \leftarrow M(Rs1 + Imm)$ (Imm: sign extended 16 bit)	I	000_100
SW Imm (Rs1), Rd	$M(Rs1 + Imm) \leftarrow Rd$	I	001_000
BEQ Rs1, Rs2, Label	Rs1 = Rs2: $PC \leftarrow PC+4+Label$ Rs1 \neq Rs2: $PC \leftarrow PC+4$	I	010_000
J Label	$PC \leftarrow PC + 4 + \text{sign_extd}(\text{imm26})$	J	001_100



Datapath for Instruction Fetch

 

Register File: A Datapath Component

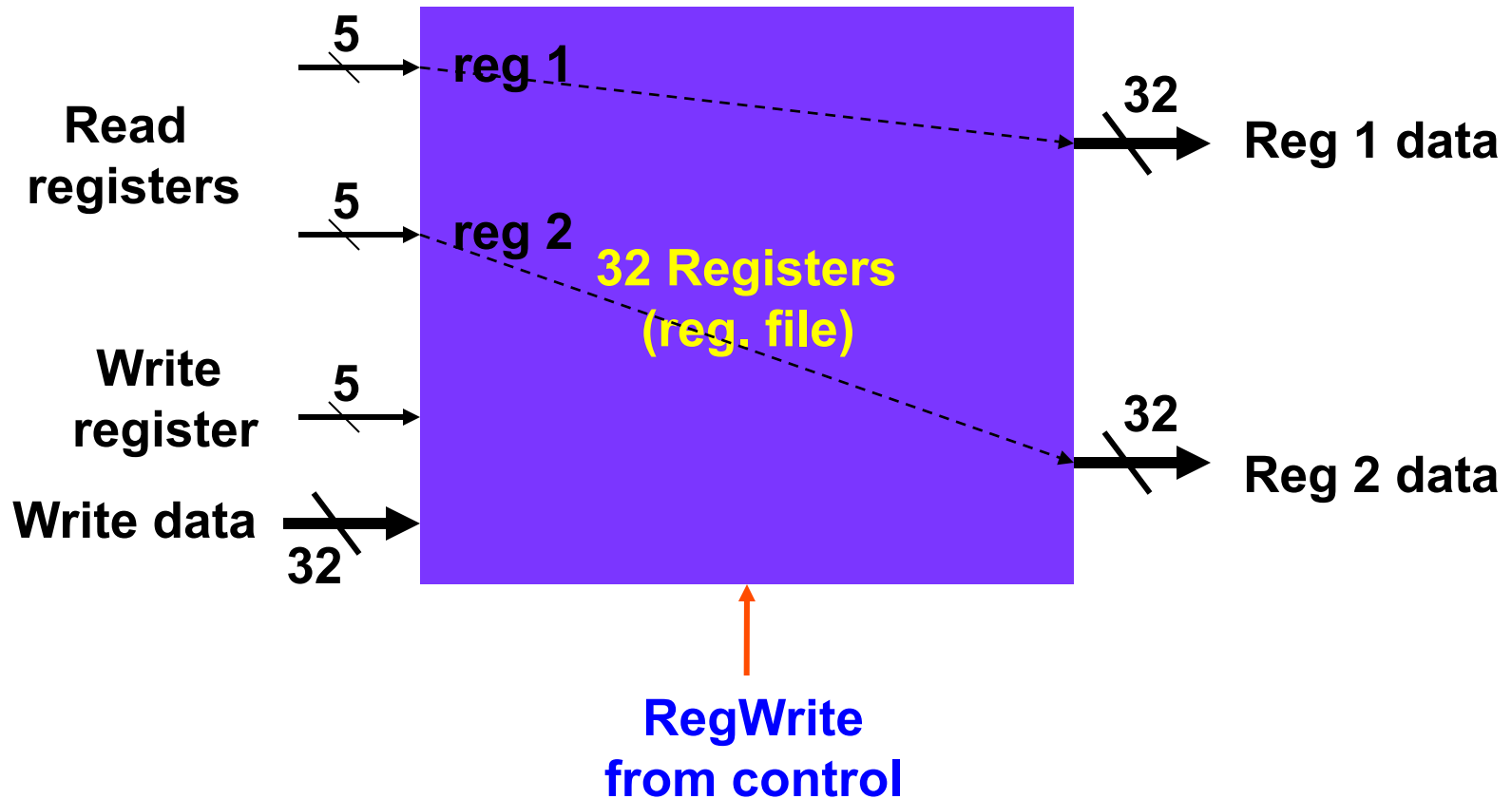

Multi-Operation ALU

Operation
select

ALU function

010

Add

011

Subtract

100


AND

101

XOR

110

Shift left

 

zero = 1, when all bits of result are 0

R-Type Instructions

- Also known as arithmetic-logical instructions
- **add, sub, and, xor, sll**
- Example: add R17, R18, R8

- Machine instruction word


000000 10001 10010 01000 00000 000100

opcode R17 R18 R8 function

- Read two registers
 - Write one register
 - Opcode and function code go to control unit that generates RegWrite and ALU operation code.



Datapath for R-Type Instruction

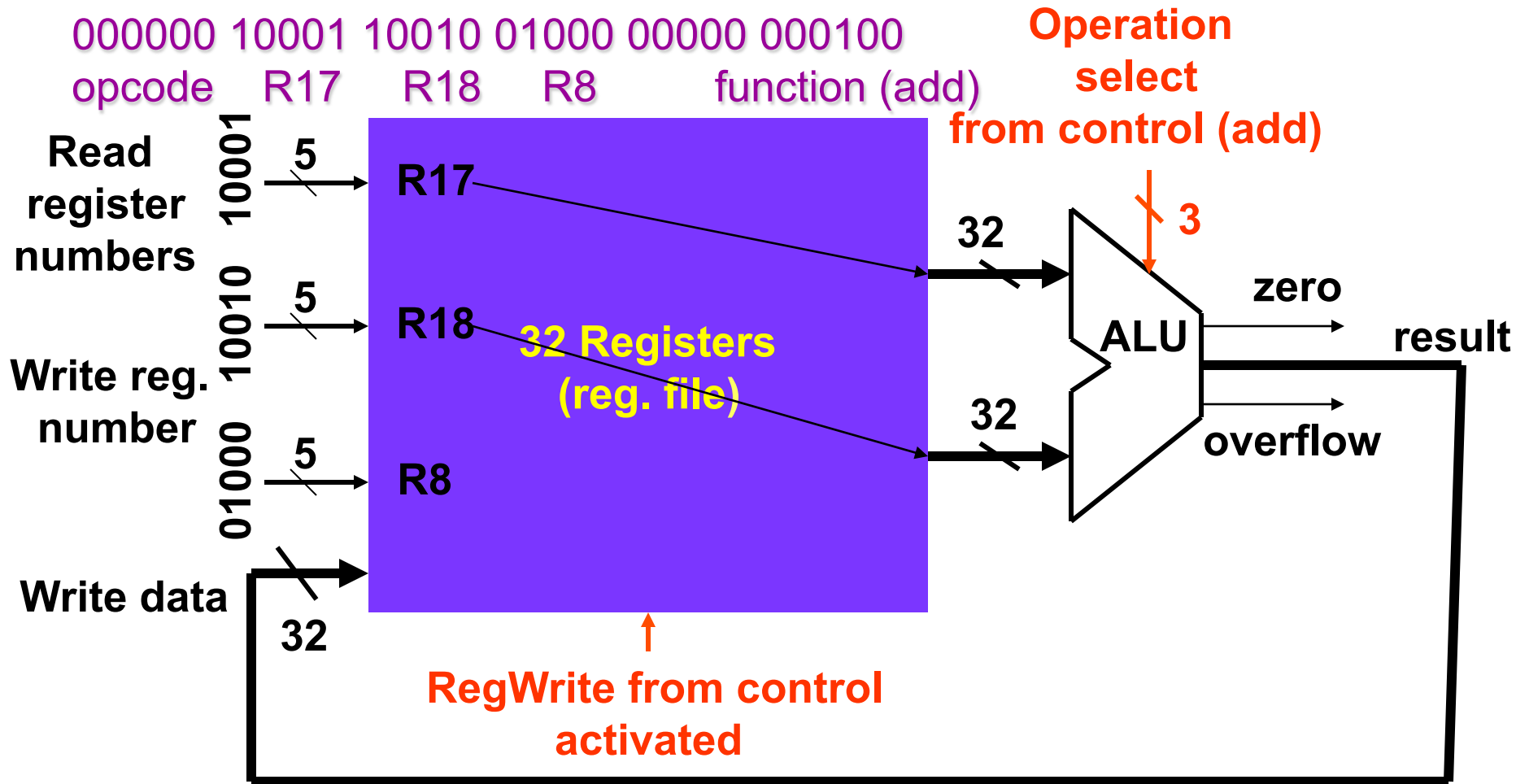

Load and Store Instructions

- l-type instructions
- **lw** R8, 1200 (R9) # incr. in bytes

000100 01001 01000 0000 0100 1011 0000
opcode R9 R8 1200


- **sw** R8, 1200 (R9) # incr. in bytes

001000 01001 01000 0000 0100 1011 0000
opcode R9 R8 1200




Datapath for **lw** Instruction

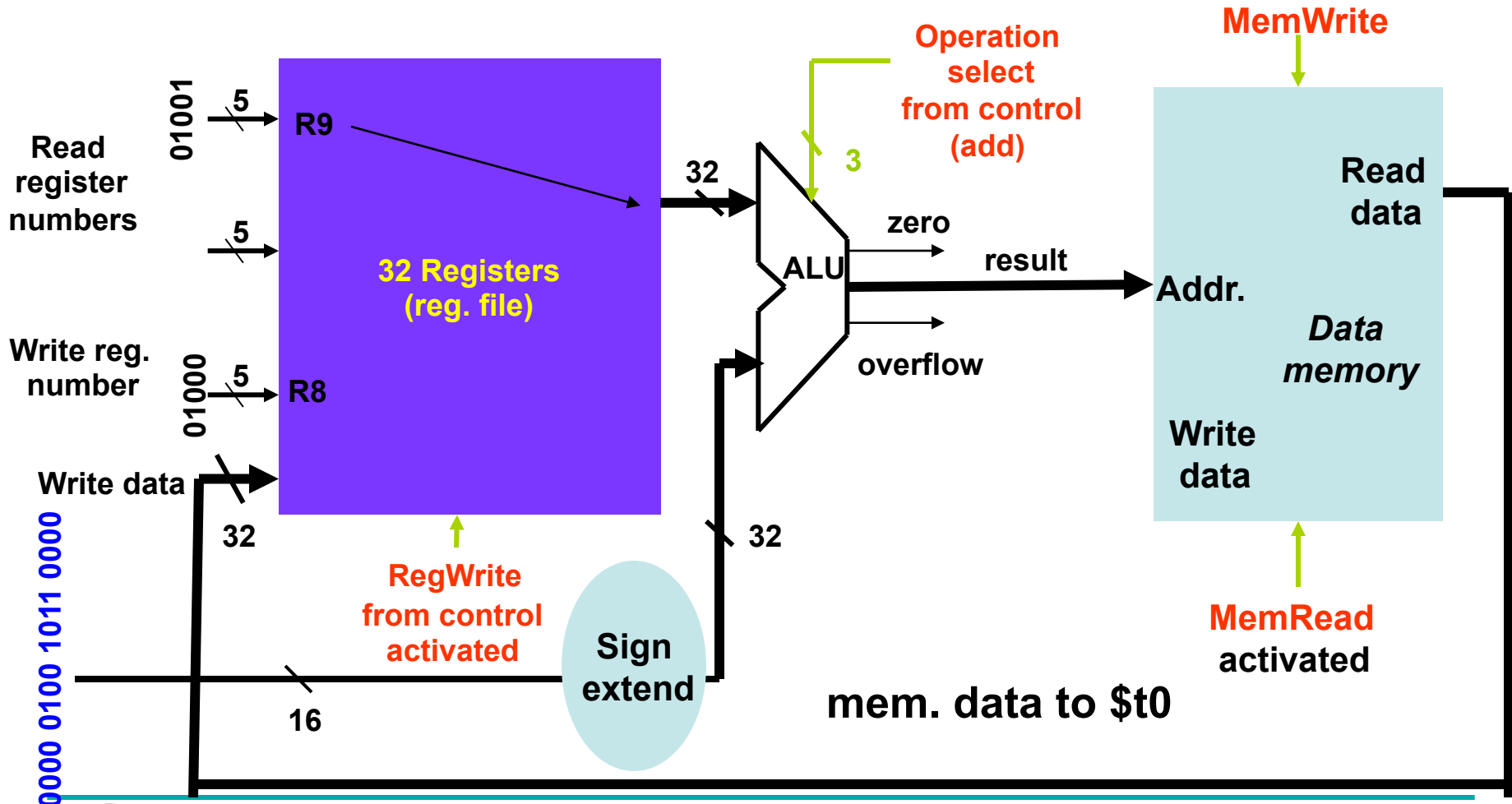000100 01001 01000 0000 0100 1011 0000
opcode R9 R8 1200



Datapath for **sw** Instruction

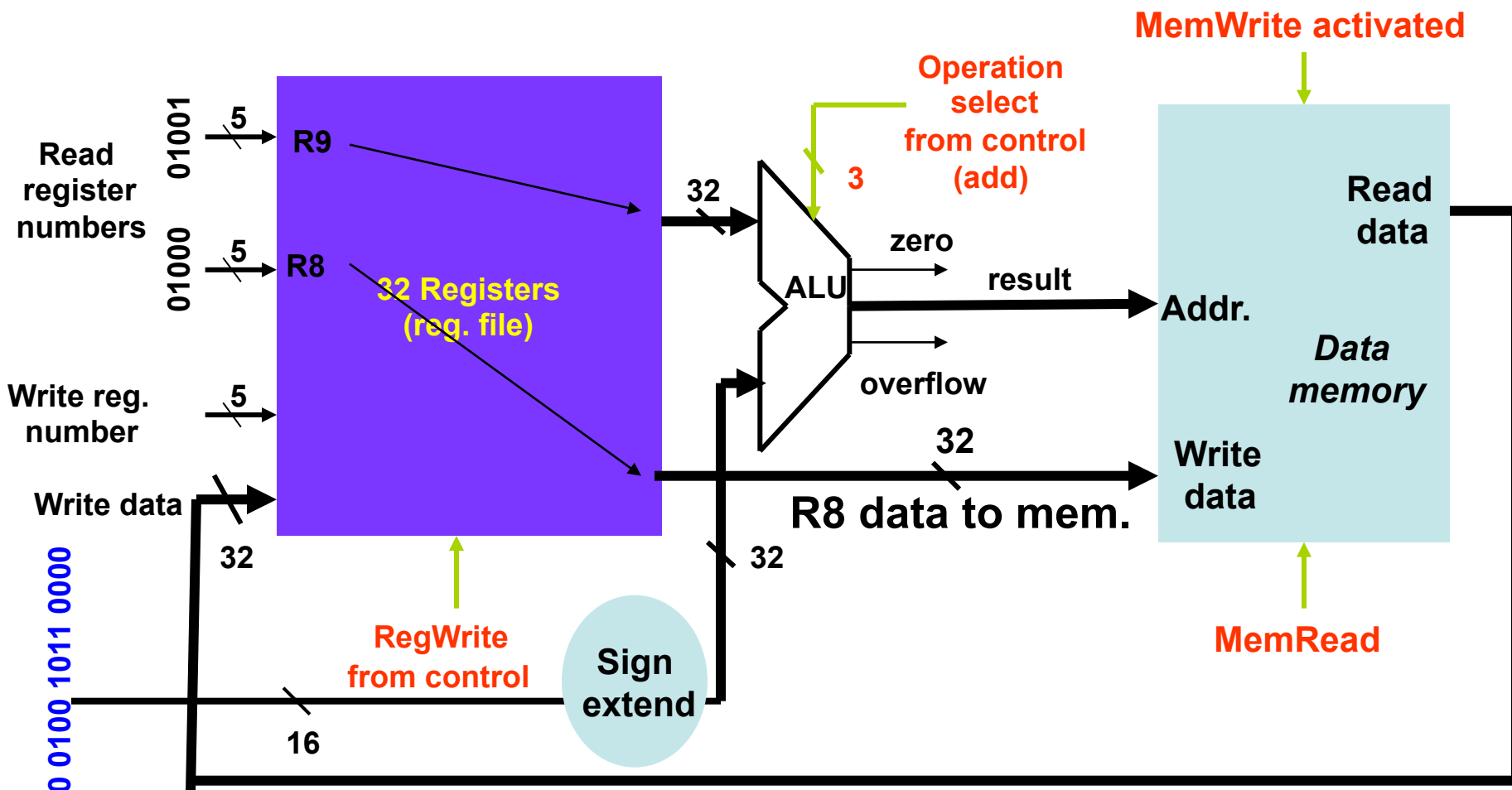001000 01001 01000 0000 0100 1011 0000
opcode \$t1 \$t0 1200




0000 0100 1011 0000



Branch Instruction (I-Type)

 
- beq R17, R18, 25 # if R17 = R18,
advance PC through
25 instructions



Note: Can branch within $\pm 2^{15}$ words from the current instruction address in PC.




Datapath for beq Instruction

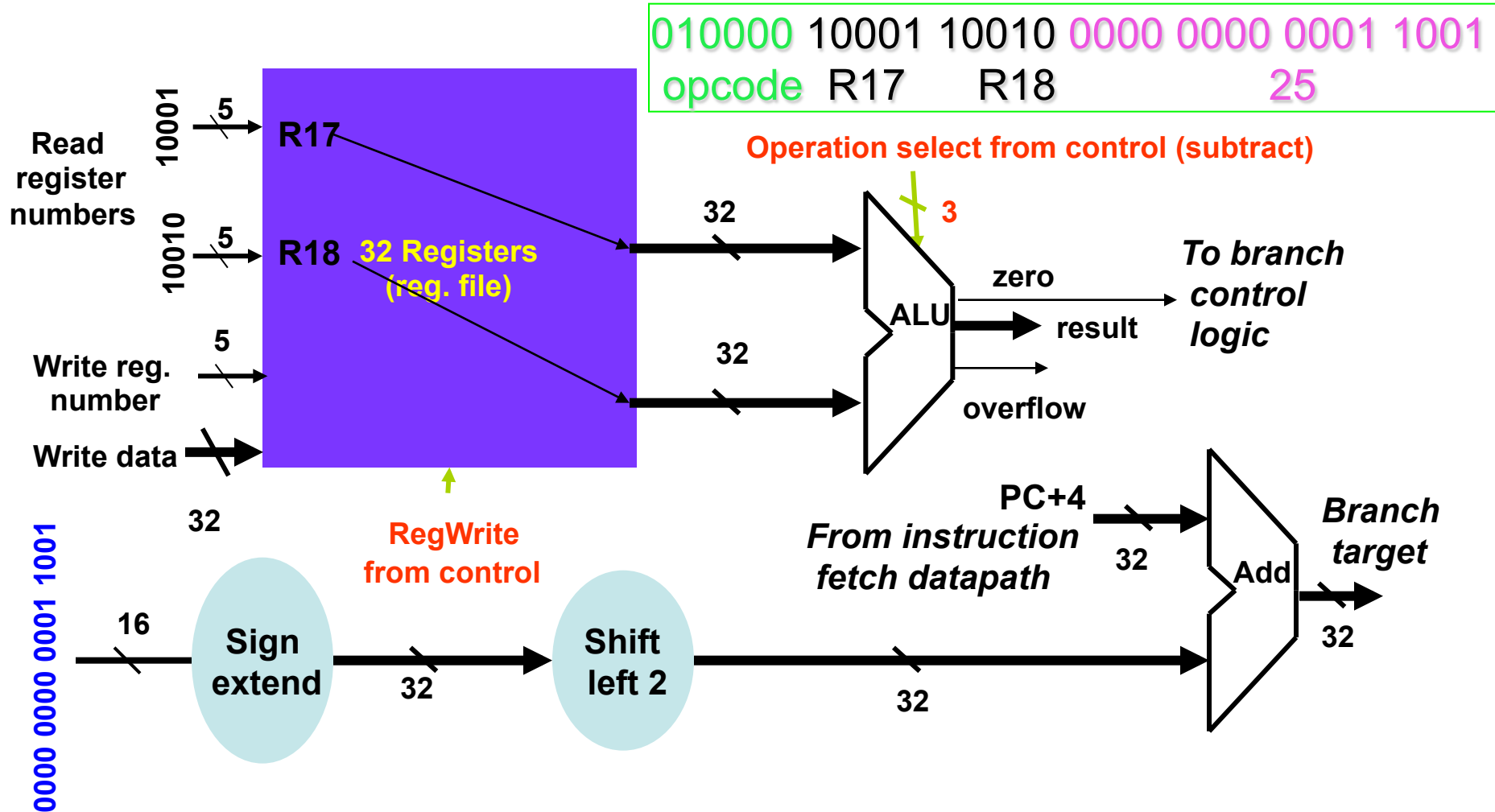


J-Type Instruction


- **j 2500** # jump to instruction 2,500

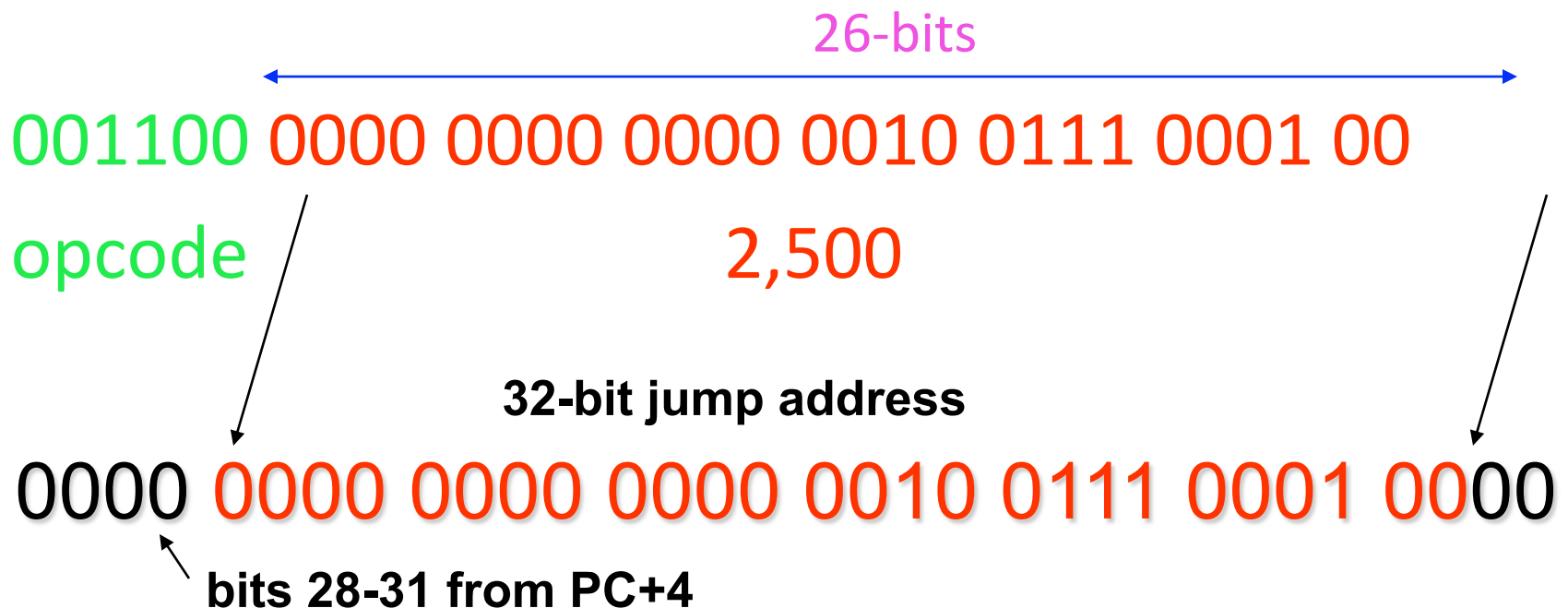


Datapath for Jump Instruction

 

Combined Datapaths

 

Control Logic

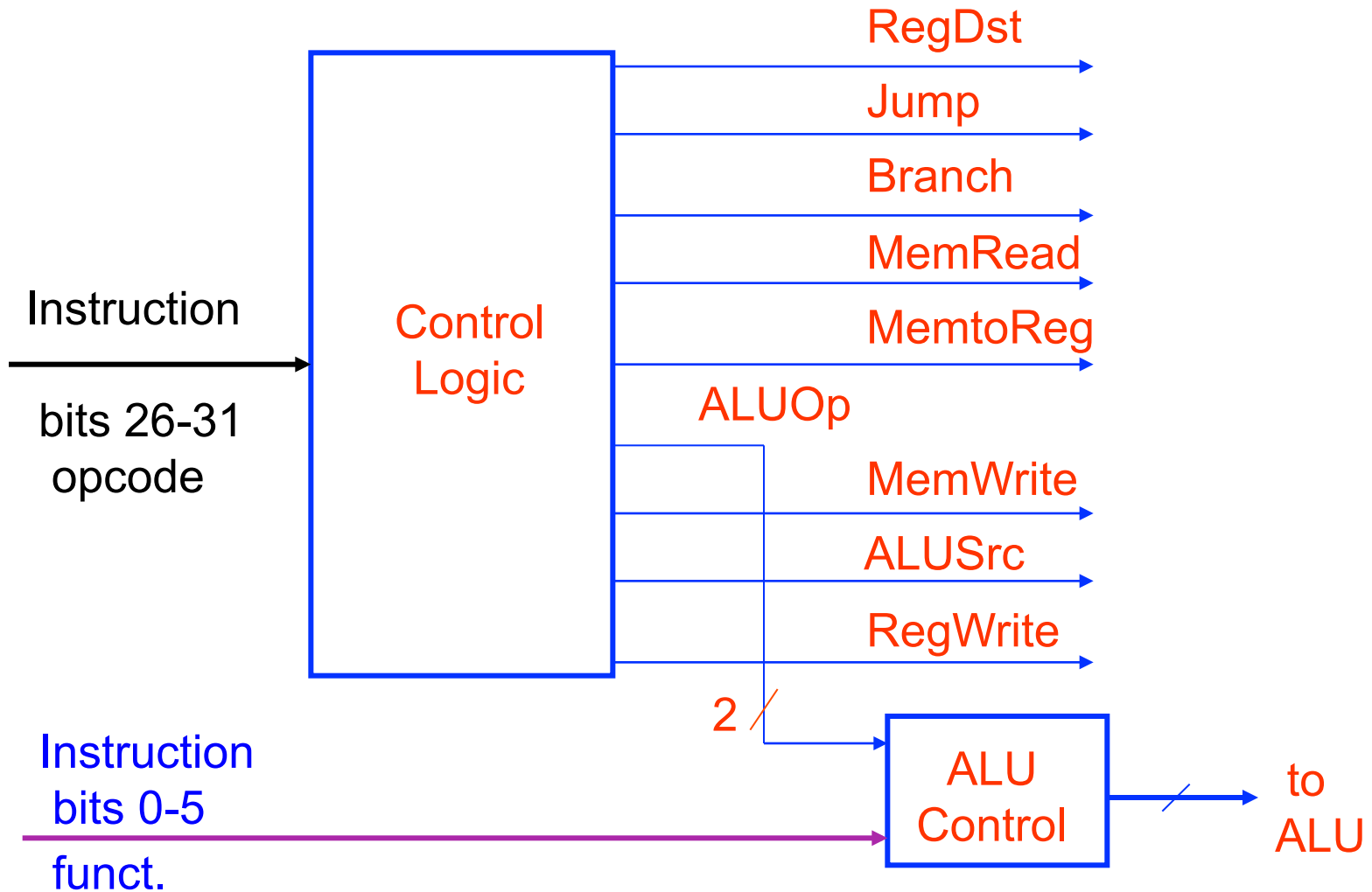

Control Logic: Truth Table

Instr type	Inputs: instr. opcode bits						Outputs: control signals									
	31	30	29	28	27	26	RegDst	Jump	ALUSrc	MemoReg	RegWrite	MemRead	MemWrite	Branch	ALOp1	ALOp2
R	0	0	0	0	0	0	1	0	0	0	1	0	0	0	1	0
lw	1	0	0	0	1	1	0	0	1	1	1	1	0	0	0	0
sw	1	0	1	0	1	1	X	0	1	X	0	0	1	0	0	0
beq	0	0	0	1	0	0	X	0	0	X	0	0	0	1	0	1
j	0	0	0	0	1	0	X	1	X	X	X	X	X	X	X	X



How Long Does It Take?

- Assume **control logic is fast** and does not affect the critical timing. Major time delay components are ALU, memory read/write, and register read/write.
- Arithmetic-type (R-type)
 - Fetch (memory read) 2ns
 - Register read 1ns
 - ALU operation 2ns
 - Register write 1ns
 - **Total 6ns**



Time for lw and sw (I-Types)

- ALU (R-type) 6ns
- Load word (I-type)
 - Fetch (memory read) 2ns
 - Register read 1ns
 - ALU operation 2ns
 - Get data (mem. Read) 2ns
 - Register write 1ns
 - Total 8ns
- Store word (no register write) 7ns



Time for beq (I-Type)

- ALU (R-type) 6ns
- Load word (I-type) 8ns
- Store word (I-type) 7ns
- Branch on equal (I-type)
 - Fetch (memory read) 2ns
 - Register read 1ns
 - ALU operation 2ns
 - Total 5ns



Time for Jump (J-Type)

- ALU (R-type) 6ns
- Load word (I-type) 8ns
- Store word (I-type) 7ns
- Branch on equal (I-type) 5ns
- Jump (J-type)
 - Fetch (memory read) 2ns
 - Total 2ns



How Fast Can the Clock Be?

- If every instruction is executed in one clock cycle, then:
 - Clock period must be at least 8ns to perform the longest instruction, i.e., $1/w$.
 - This is a single cycle machine ($CPI = 1$)
 - It is slower because many instructions take less than 8ns but are still allowed that much time.
- Method of speeding up: Use multicycle datapath.



Thank You

