
8051 Microcontroller: Interfacing

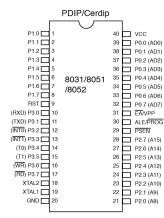

Virendra Singh

Computer Architecture and Dependable Systems Lab
Department of Electrical Engineering
Indian Institute of Technology Bombay
http://www.ee.iitb.ac.in/~viren/


Ė-mail: viren@ee.iitb.ac.in

FE-309: Microprocessors







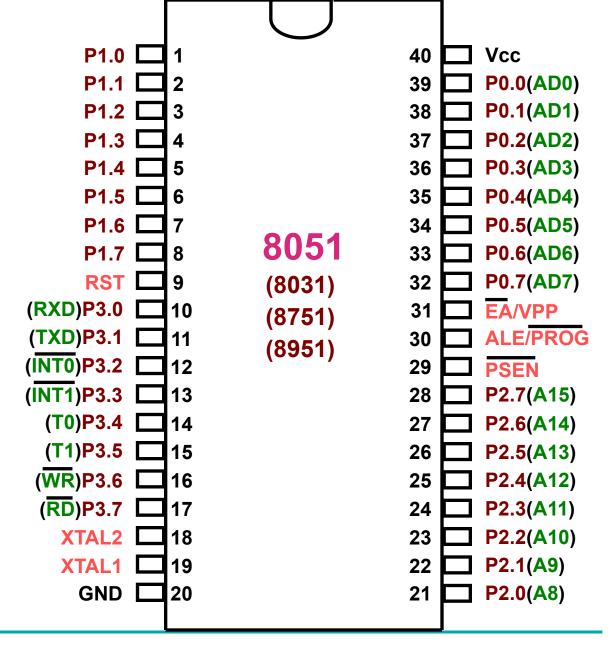



CADSL

2

I/O Devices (Peripherals)

- Examples: switches, LED, LCD, printers, keyboard etc.
- Interface chips
 - are needed to resolve the speed problem
 - synchronizes data transfer between CPU and I/O device
- Connection of Interface and CPU
 - Data pins are connected to CPU data bus
 - I/O port pins are connected to I/O device
- CPU may be connected to multiple interface
- IO ports are simplest interface





I/O Interfacing

 Dedicated instructions for IO operations (Isolated I/O)

 Same instruction for memory and IO (memory-mapped I/O)

8051 is memory mapped






Keyboard Interfacing





Interfacing Switches

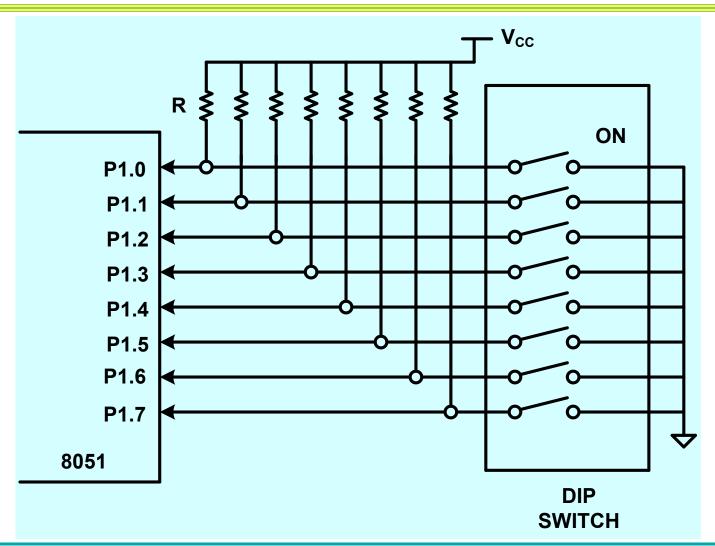






Interfacing Keyboard

- Collection of keys interfaced to the microcontroller
- Arranged in the form of two dimensional matrix
- Matrix arrangement used for minimizing the number of port lines
- Junction of each row and column forms the key





Interfacing a Keyboard

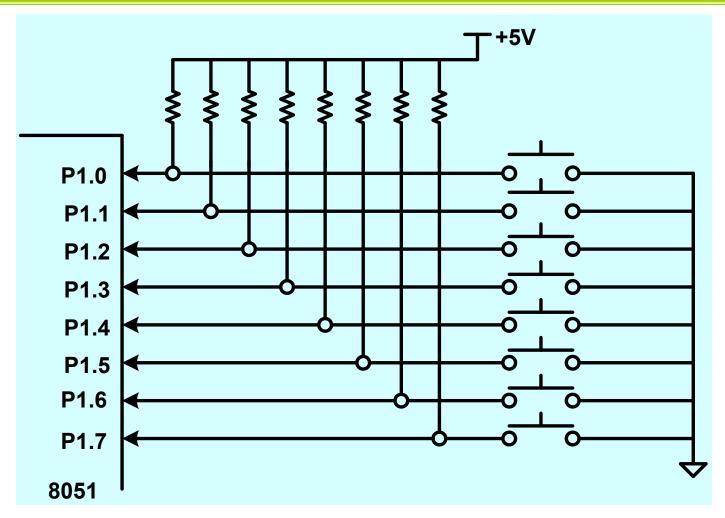


➤ One key per port line





Interfacing a Keyboard

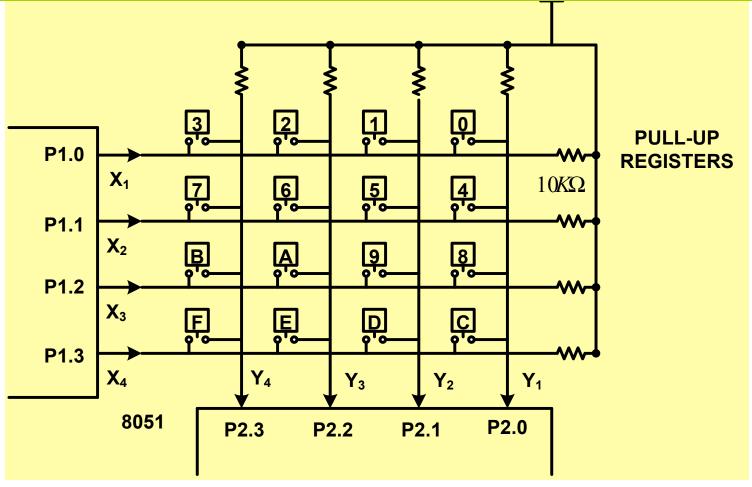


Keys are organized in two-dimensional matrix to minimize the number of ports required for interfacing





Interfacing a Keyboard

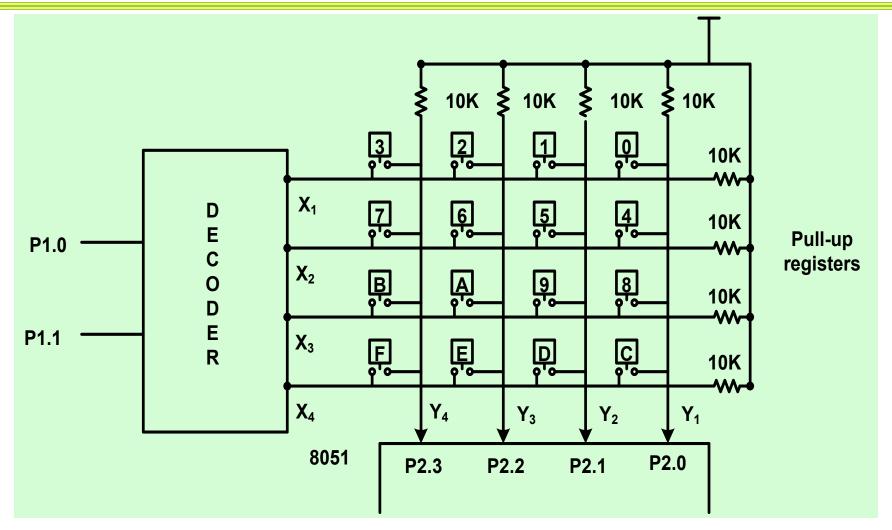

Use of decoder further reduces the number of port lines required



Key Issues in Keyboard Interfacing

- Key bounce can be overcome using Software/Hardware approach
- Keyboard Scanning
- Multiple Key Closure

- Minimize Hardware Requirement:
 - Use of Keyboard Encoder
- Minimize Software Overhead





Thank You



