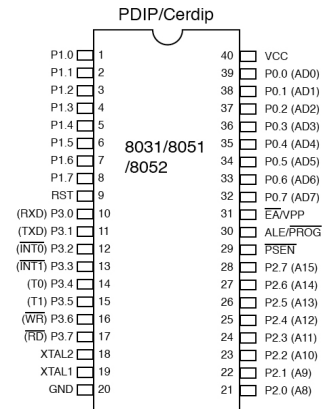


8051 Microcontroller: Interfacing



Virendra Singh

Computer Architecture and Dependable Systems Lab

Department of Electrical Engineering
Indian Institute of Technology Bombay

<http://www.ee.iitb.ac.in/~viren/>

E-mail: viren@ee.iitb.ac.in


EE-309: Microprocessors



Lecture 13 (17 Aug 2015)

CADSL


8051 Pin Diagram

 

Keyboard Interfacing




Interfacing a Keyboard

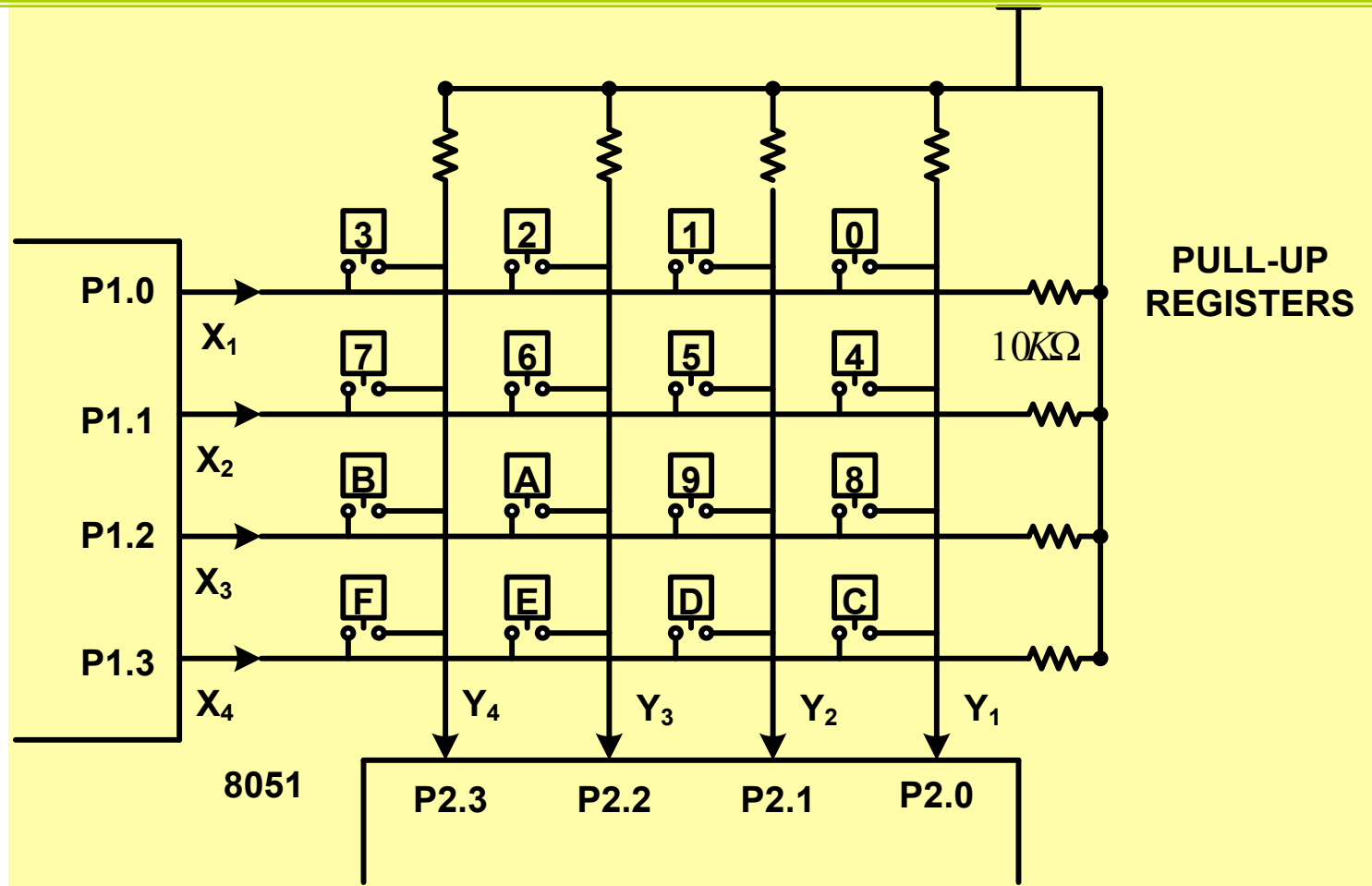

- Keys are organized in two-dimensional matrix to minimize the number of **ports** required for interfacing

Interfacing a Keyboard

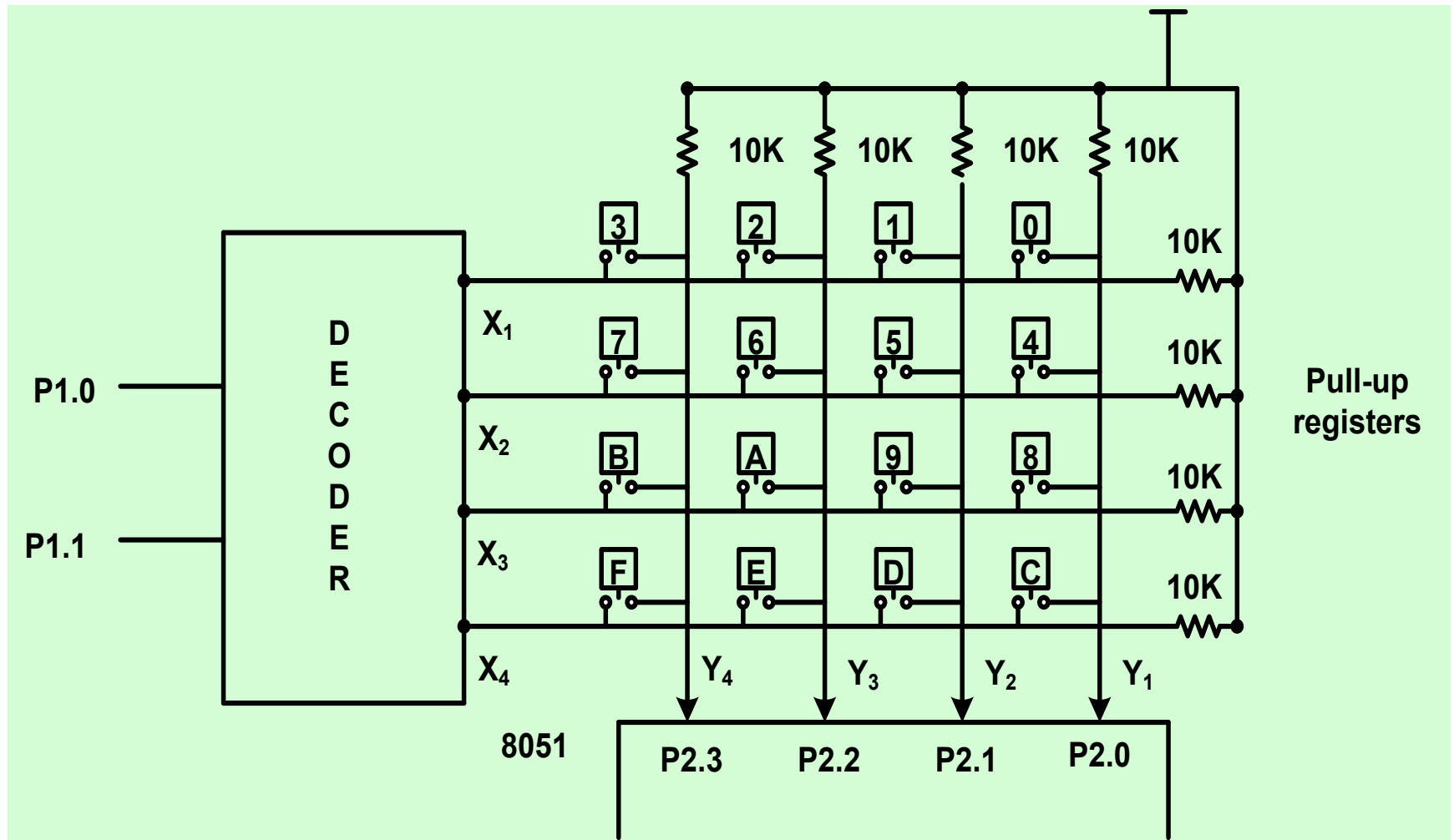


➤ Use of decoder further reduces the number of port lines required

Key Issues in Keyboard Interfacing

- Key bounce can be overcome using Software/Hardware approach
- Keyboard Scanning
- Multiple Key Closure
- Minimize Hardware Requirement:
 - Use of Keyboard Encoder
- Minimize Software Overhead




Key Bounce

 

➤ Hardware approach to overcome key-bounce


Keyboard Scanning

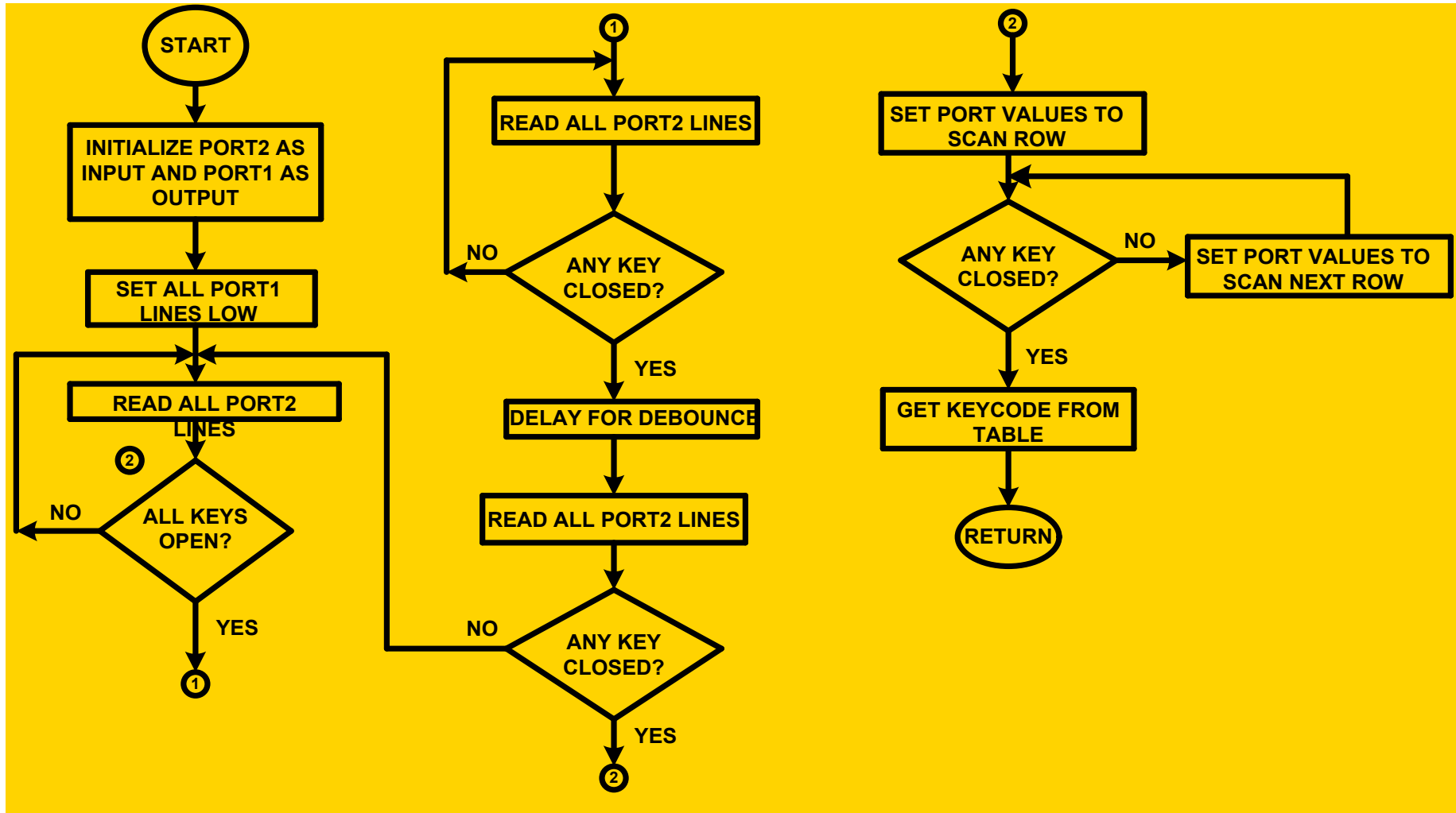

➤ Software approach for keyboard scanning

Keyboard Scanning

 - Send ASCII code for pressed key
- P1.0 – P1.3 connected to rows as output port
- P2.0 - P2.3 connected to columns as input port



	MOV P2, #0FFH	; P2 as input port
K1:	MOV P1, #00H	; Ground all rows at once
	MOV A, P2	; Read all columns
		; Ensure all keys are open
	ANL A, #0000 1111B	; mask unused bits
	CJNE A, #0000 1111B, K1	; Till all keys released



Keyboard Scanning

K2: ACALL DELAY ; call 20 ms delay
 MOV A, P2 ; see if any key is pressed
 ANL A, #0000 1111B ; mask unused bits
 CJNE A, #0000 1111B, Over ; key pressed, find row
 SJMP K2 ; check till key is pressed


Over: ACALL DELAY ; call 20 ms delay (debounce)
 MOV A, P2 ; check key closure
 ANL A, #0000 1111B ; mask unused bits
 CJNE A, #0000 1111B, Final ; key pressed find row
 SJMP K2 ; if none, keep polling



Keyboard Scanning

Final: MOV P1, #1111 1110B
MOV A, P2
ANL A, #0000 1111B
CJNE A, #0000 1111B, Row0
MOV P1, #1111 1101B
MOV A, P2
ANL A, #0000 1111B
CJNE A, #0000 1111B, Row1
MOV P1, #1111 1011B
MOV A, P2
ANL A, #0000 1111B
CJNE A, #0000 1111B, Row2

 ; Ground row 0
; Read all columns
; mask unused bits
; key row 0, find column
; Ground row 1
; Read all columns
; mask unused bits
; key row 1, find column



Keyboard Scanning


MOV P1, #1111 0111B ; Ground row 3
MOV A, P2 ; Read all columns
ANL A, #0000 1111B ; mask unused bits
CJNE A, #0000 1111B, Row3 ; key row 3, find column
LJMP K2 ; if none, false input

; Repeat

Row0: MOV DPTR, #KCODE0 ; Set DPTR at start of row 0
SJMP Find ; Find column

Row1: MOV DPTR, #KCODE1 ; Set DPTR at start of row 1
SJMP Find ; Find column

 Row2: MOV DPTR, #KCODE2 ; Set DPTR at start of row 2
SJMP Find ; Find column



Keyboard Scanning

Row3: MOV DPTR,#KCODE3 ; Set DPTR at start of row 0

Find: RRC A ; See if any CY bit is low
JNC Match ; if 0, get ASCII code
INC DPTR ; point to the next column addr
SJMP Find ; Keep searching

Match: CLR A ; Clear A, match found
MOVC A, @A+DPTR ; Get ASCII from the table
MOV P0, A ; Display pressed key
LJMP K1



Keyboard Scanning

- ASCII Lookup table for each row

```
                ORG    300H
KCODE0:         DB     '0', '1' , '2' , '3'           ; Row 0
KCODE1:         DB     '4' , '5' , '6' , '7'           ; Row 1
KCODE2:         DB     '8' , '9' , 'A' , 'B'           ; Row 2
KCODE3:         DB     'C' , 'D' , 'E' , 'F'           : Row 3
                END
```





Hardware Approach

- Use of an Encoder
- Automatically translates key press code into 4-bit number
- Built-in scanning circuit
- Overcomes key bounce using a single capacitor (1 μ F for debounce time of 10 msec)
- Keyclosure indicated by an output (DA) line
- Last key pressed is stored in a latch
- Examples of Encoder
 - 20 key encoder – 74C923
 - 16 key encoder - 74C922



Scanning by Hardware

  

- Minimizes software overhead at the expense of extra hardware

SWITCH CLOSED	DATA OUTPUT			
	D	C	B	A
Y ₁ X ₁	0	0	0	0
Y ₁ X ₂	0	0	0	1
Y ₁ X ₃	0	0	1	0
Y ₁ X ₄	0	0	1	1
Y ₂ Y ₁	0	1	0	0
Y ₂ Y ₂	0	1	0	1
Y ₂ Y ₃	0	1	1	0
Y ₂ Y ₄	0	1	1	1
⋮				
Y ₄ X ₄	1	1	1	1

Display Interfacing






Display Devices

- Most popular display device: LED
 - Very tiny in size
 - Available in many colors
 - Very reliable and rugged
 - Long life
 - Operates at low voltage
 - Small power consumption
 - Visible in darkness
- Single LED
- Seven Segment Displays
 - Common Cathode Form (ICM 7218D)
 - Common Anode Form (ICM 7218C)
- Consumes large amount of current






Interfacing a single LED

   
➤ Driver circuit to interface a single LED




Seven Segment LEDs

 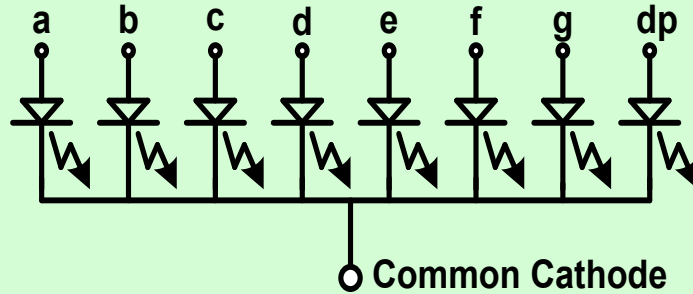 

 - Two types: Common cathode and common anode type
- Seven-segment LEDs can be conveniently used to display HEX characters



Interfacing multiple 7-Segment LEDs

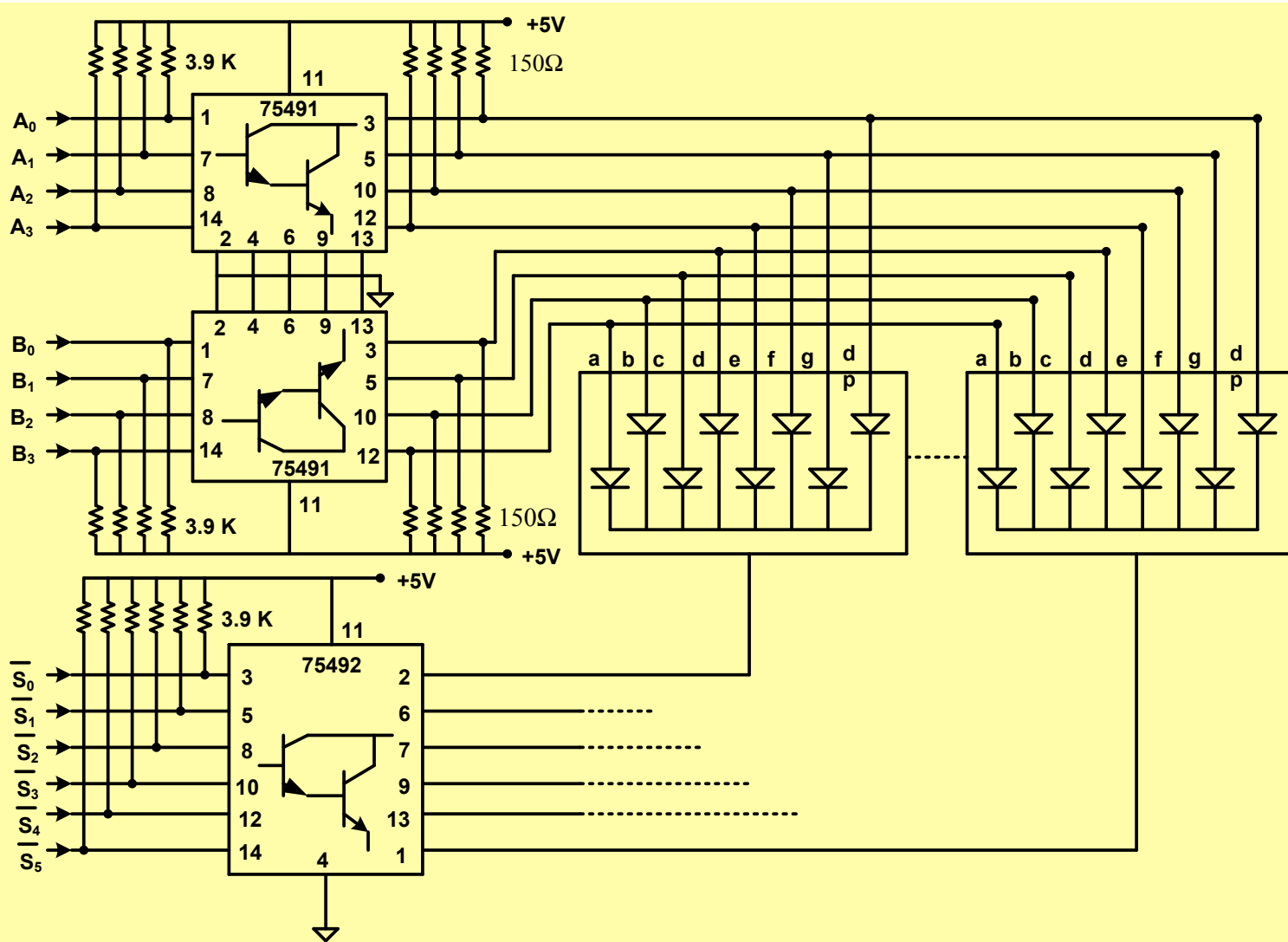


Multidigit Driver

- Features of Multidigit Driver
 - 8-segment driver output lines
 - 8-digit driver lines
 - 20 mA peak current
 - LEDs can withstand high peak current
- Sequencing operation:
 - Select data using digit address lines DA_{0-2}
 - Write data using ID_{0-3} and ID_7 lines
- Three modes of operation:
 - HIGH: HEX, LOW: OFF, OPEN: CODED-HELP



Interfacing using Multidigit Driver

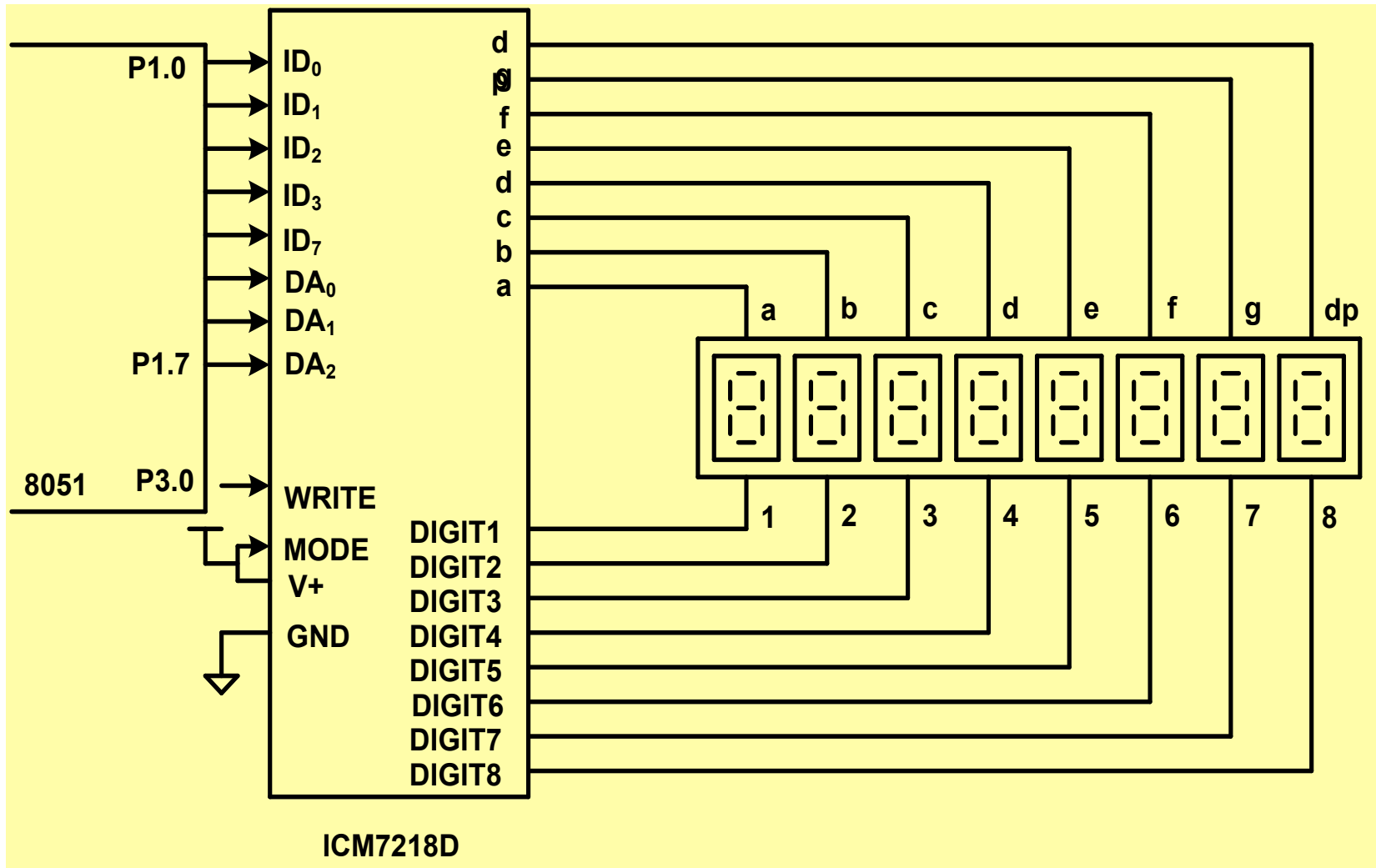


Data Communication



8051 and PC

 - The 8051 module connects to PC by using RS232.
- RS232 is a protocol which supports half-duplex, synchronous/asynchronous, serial communication.



Simplex vs. Duplex Transmission

- **Simplex transmission:** the data can sent in one direction.
 - Example: the computer only sends data to the printer.




- **Duplex transmission:** the data can be transmitted and receive




Half vs. Full Duplex

 - **Half duplex**: if the data is transmitted one way at a time.




 - **Full duplex**: if the data can go both ways at the same time.
 - Two wire conductors for the data lines.




Simplex, Half-, and Full-Duplex Transfers

Half Duplex

 

Full Duplex

 


Parallel vs. Serial Data Transfer

- Computers transfer data in two ways:
 - Parallel
 - data is sent a byte or more a time (fast)
 - Only short distance between two systems
 - The 8-bit data path is expensive
 - Example: printer, hard disks
 - Serial
 - The data is sent one bit at a time (slow)
 - Long distance (rarely distortion)
 - cheap
 - The data can be transferred on the telephone line (by using modem.)




Serial vs Parallel Data Transfer

Serial Transfer

 


Parallel Transfer

 


Serial vs. Parallel Data Transfer

Serial Transfer

 

Other control lines

Parallel Transfer

 

Other control lines

Serial Communication


- How to transfer data?

- Sender:

- The byte of data must be converted to serial bits using a parallel-in-serial-out shift register.
 - The bit is transmitted over a single data line.


- Receiver

 - The receiver must be a serial-in-parallel-out shift register to receive the serial data and pack them into a byte.




Asynchronous vs. Synchronous

 - Serial communication uses two methods:
 - In synchronous communication, data is sent in blocks of bytes.



 - In asynchronous communication, data is sent in bytes.



UART and USART

- It is possible to write software to use both methods, but the programs can be tedious and long.
- Special IC chips are made for serial communication:
 - USART (universal synchronous-asynchronous receiver-transmitter)
 - UART (universal asynchronous receiver-transmitter)
- The 8051 chip has a built-in UART.



Thank You

