ME 310: Microprocessors and Automatic Control Lab

Fundes: How to run motor? Encoder interfacing



P.S. Gandhi Mechanical Engineering IIT Bombay

PRASANNA S GANDHI gandhi@me.iitb.ac.in



Goal: Feedback control of motor

- What is that we have seen so far
 - Fundes about Flipflop and programing microprocessor interfaces: Digital input output interface, PWM
 - How to run motor using microprocessor
- Q: what we should use as feedback for the closed loop? Any ideas!!
- Position sensing by what means?

PRASANNA S GANDHI gandhi@me.iitb.ac.in


2



Position sensing

- Sensors and interfaces to sense position
 - Potentiometer: interface required ADC
 - Encoder: interface PWM and Digital i/o
- Advantages and disadvantages of these
 - Potentiometer: analog: noisy data, limited range (10 turn)
 - Encoder: digital, clean signal, limited by number overflow but software correction can be done.


How encoder works?

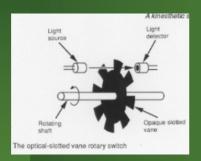



- Source light is cut by the toothed/slits disc
- Signal from photodiode gives pulses that can be counted
- Q: How to detect direction of motion?


PRASANNA S GANDHI gandhi@me.iitb.ac.in


.

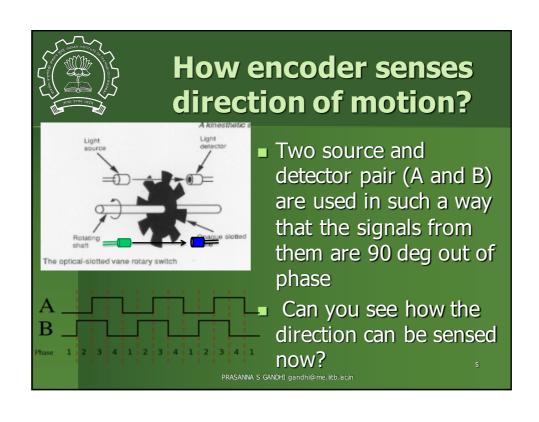


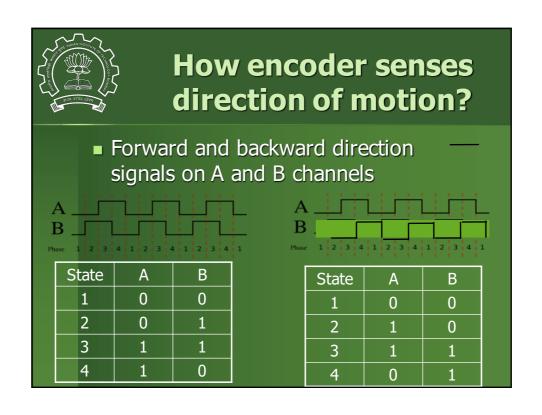


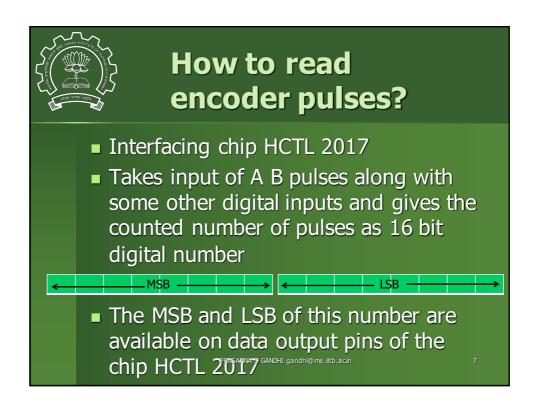


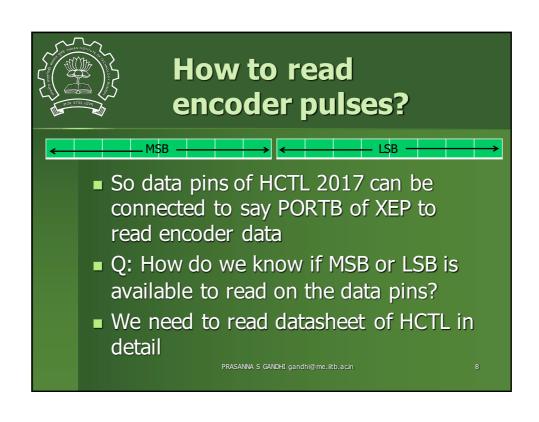

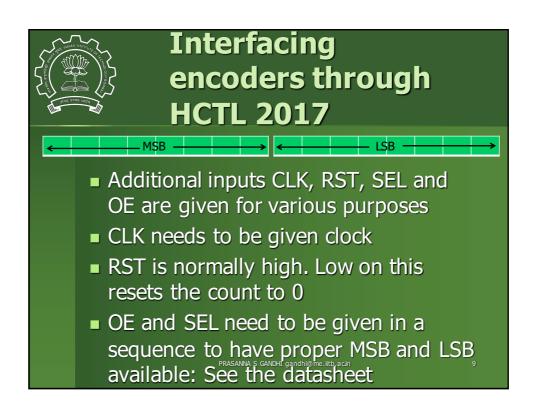

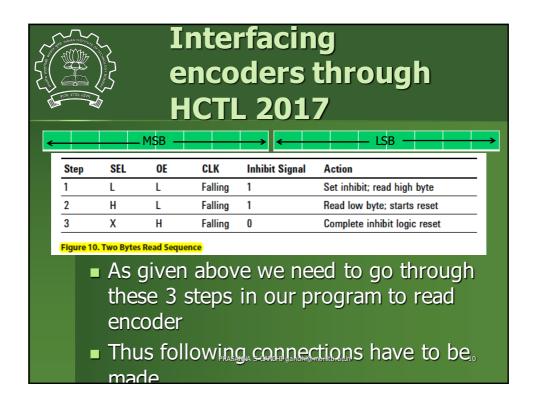

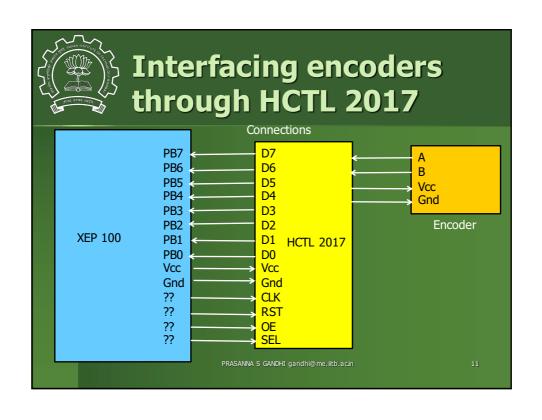

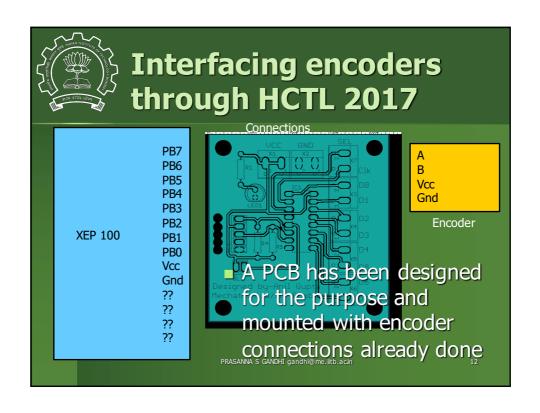







Program

- Clock input to HCTL is provided using PWM signal
- See the program in handout and identify connections to be made
- Follow the handout

PRASANNA S GANDHI gandhi@me.iitb.ac.in

14

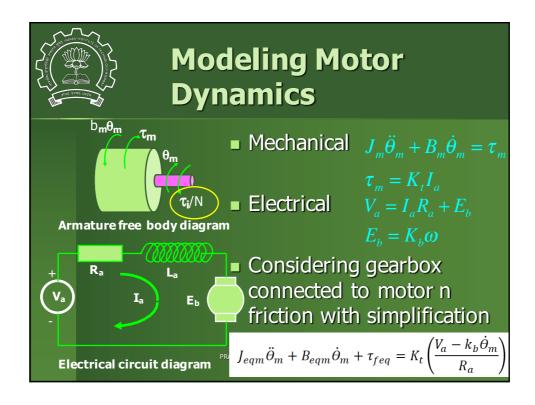

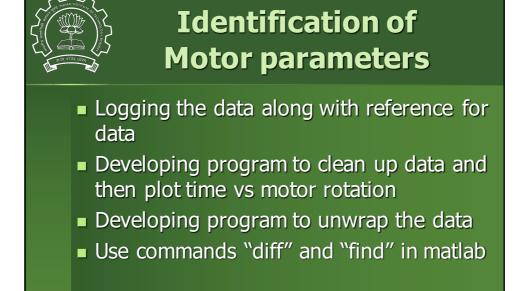

PRASANNA S GANDHI gandhi@me.iitb.ac.in

